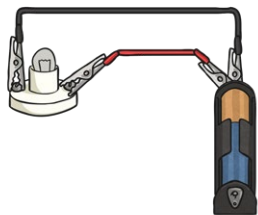
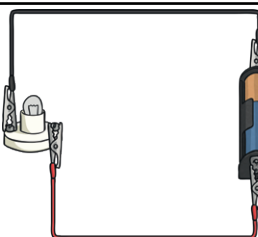
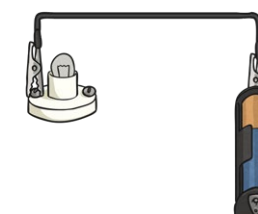
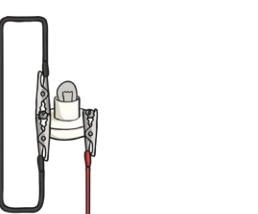


# Complete and Incomplete Circuits Answers

Circuit	Complete or Incomplete?
	Incomplete
	Complete
	Incomplete
	Incomplete

What is the difference between the complete and incomplete circuits?

**The complete circuit has:**

1. A power supply (the battery).
2. No gaps anywhere, so the electrical current can flow around the entire circuit.
3. The wires connecting to both the positive and negative ends of the battery.

**The incomplete circuits have either one of the following problems, or both:**

1. A gap in the circuit, so the electrical current cannot flow around it.
2. Wires that do not connect to the positive and negative ends of the power supply (the battery).